 


EE5311: Digital IC Design

Tutorial 6 - Inverter layout and post-layout simulation


Skywater 130nm layer stack

(Diagram not to scale!)



Layout Rules - Rudimentary Design Rule Checks (DRC)

 - Basic DRCs that will get you an *almost* DRC clean layout:



- Exhaustive list of DRCs:

<https://skywater-pdk.readthedocs.io/en/main/rules/periphery.html>

Layers and DRCs


PDK layer	KLayout layer	Purpose	Min. width (μm)	Min. spacing (μm)	Min. area (μm^2)
nwell	nwell.drawing	N-well for pMOS	0.84	1.27	–
diffusion	diff.drawing	Source/Drain diffusion for n/p-MOS	0.15	0.27	0.265(n) 0.255(p)
polysilicon	poly.drawing	Polysilicon gate	0.15	0.21	–
licon	licon1.drawing	via between diff/poly li	0.17	0.17	–
li	li1.drawing	local interconnect	0.17	0.17	0.0561
mcon	mcon.drawing	via between li and metal1	0.17	0.19	–
metal1	met1.drawing	Metal-1 routing layer	0.14	0.14	0.083
via1	via.drawing	via between metal1 and metal2	0.15	0.17	–
metal2	met2.drawing	Metal-2 routing layer	0.14	0.14	0.0676
via2	via.drawing	via between metal2 and metal3	0.20	0.20	–
metal3	met3.drawing	Metal-3 routing layer	0.30	0.30	0.240
via3	via.drawing	via between metal3 and metal4	0.20	0.20	–
metal4	met4.drawing	Metal-4 routing layer	0.30	0.30	0.240
via4	via.drawing	via between metal4 and metal5	0.80	0.80	–
metal5	met5.drawing	Metal-5 routing layer	1.60	1.60	4.000

Layers and DRCs ...


Via layer	Adjacent layer	Min. enclosure (μm) (values on the adjacent edges of the enclosing metal)
licon	diffusion	0.06/0.06
licon	poly	0.05/0.08
licon	li	0.08/0.08
mcon	li	0.00/0.00
mcon	metal1	0.03/0.06
via1	metal1	0.055/0.085
via1	metal2	0.055/0.085
via2	metal2	0.040/0.085
via2	metal3	0.065/0.065
via3	metal3	0.06/0.09
via3	metal4	0.065/0.065
via4	metal4	0.19/0.19
via4	metal5	0.31/0.31

Inverter schematic

 - Use the pfet_01v8 and nfet_01v8 devices to construct an inverter as shown below
- Use DVDD and DGND signals to connect to p/nMOS bulk and source terminals instead of the global VDD and GND signals.



Measure delay of the inverter

 


KLayout - setup, invocation and shortcuts

- Before invoking klayout for the first time execute the command `source /cad/setup/layout_init.sh`. *Execute this only once.*
- Invoke klayout in edit mode using: `klayout -e`
- Shortcuts:

Function	Shortcut
Create an instance	i
Create a box on the selected layer	b
Stretch an edge of a polygon/rectangle	s
Select an object	Left mouse click
Move	m
Copy	c
Paste interactively	p
Insert a label	l
Draw ruler	k
Clear rulers	Ctrl k
Object properties	q
Save layout	Ctrl s
View all hierarchy	*
Undo	Ctrl z
Redo	Ctrl y


New layout

 - Create a new layout in KLayout using File ► New layout
- Name the top cell as `inv` as shown below




Select tap

 - Choose the `custom_sky130.gds` in the Libraries list as below:




Insert tap

 - Insert the `tap` cell by dragging and dropping it onto the canvas
- Press `*` to show the contents of tap cell
- Top and bottom `met1.drawing` shapes connect the `nWell` and `pSubstrate` to the `DVDD` and `DGND` signals respectively
- The tap cell serves as the reference height for your standard cells




Extend power lines

 - Extend the power and ground lines by drawing boxes on `met1.drawing` layer using the shortcut key: `b`




Insert pfet

 - Switch to the sky130 Pcells library in the Libraries list
- Insert a pfet by dragging and dropping it on canvas
- Modify the PCell parameters `width = 0.84`
- Insert the pfet such that its `nwell` abuts the `nwell` of tap




Insert nfet

 - Insert a `nfet` by dragging and dropping it on canvas
- Insert the `nfet` such that its `poly` aligns with that of `pfet`
- Use the ruler (shortcut `k`) to align the polys




Connect polys

 - Connect the `nfet` and `pfet` polys using a box on the `poly.drawing` layer (shortcut: `b`)




Connect drains

 - Connect the `nfet` and `pfet` drains using a box on the `li1.drawing` layer (shortcut: `b`)
- Insert a via from the `poly` to `li` using the Pcell `vias_gen`




Connect sources to power and ground

 - Connect p_{fet} source to the top metal using a box on the li1 layer and a via from the li to metal using the vias_gen
- Connect n_{fet} source to the bottom metal similarly




Unhide empty layers

 - Unhide the empty layers by right clicking on the layers box and unchecking the checkbox shown below:




Insert labels

 - Insert the labels `in` and `out` on the `li1.label` layer on the poly and diffusion contacts respectively (shortcut: 1)
- Insert the labels `DVDD` and `DGND` on the `met1.label` layer on the top and bottom `met1` drawings.




DRC, LVS and Extraction

 - Run DRC using: Efabless sky130 ► Run Magic DRC
- Run LVS using: Efabless sky130 ► Run Magic LVS
- If you get any DRC/LVS errors fix them until there are none.
- Run Extract using: Efabless sky130 ► Run Magic Extract
- Post layout extracted netlist will be saved as: inv_extracted.spice



Post-layout simulation: Modify inverter symbol

 To prevent `xscem` from netlisting the inverter, modify the symbol type from subcircuit to primitive as shown below:



Post-layout simulation: Measure delay of the inverter

Include the extracted netlist as shown below and find the delay of the inverter post-layout.

